

EXPERIMENT 1

Digital to Analog (DAC) Conversion

OBJECTIVE

Purpose of the experiment is to obtain analog voltage and/or current from digital signal.

EQUIPMENT REQUIRED

Components

- 1*LF351 OPAMP
- 5*20K Ω
- 15*10K Ω
- 4*switch

PRELIMINARY WORK

Study OPAMP summing amplifiers and review how to use it as a Digital to Analog Converter (DAC) by binary weighted resistors and R-2R ladder arrangement.

BACKGROUND INFORMATION

A digital to analog converter (DAC) converts a digital signal to an analog voltage or current output. Many types of DACs are available and usually switches, resistors, and op-amps are used to implement the conversion. In Figure 1, a summing amplifier with binary weighted resistors are given.

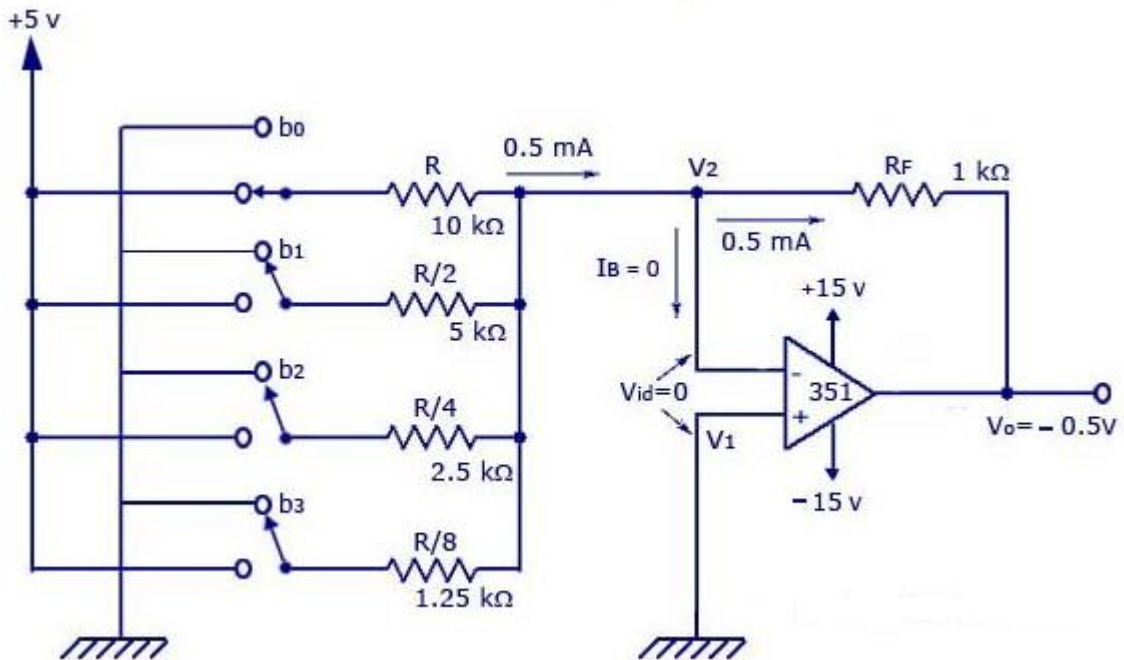


Figure 1. DAC by opamp summing amplifier with binary weighted resistors

R-2R Ladder is another type of DAC based on the opamp summing amplifier similarly as seen in Figure 2. Each bit corresponds to a switch:

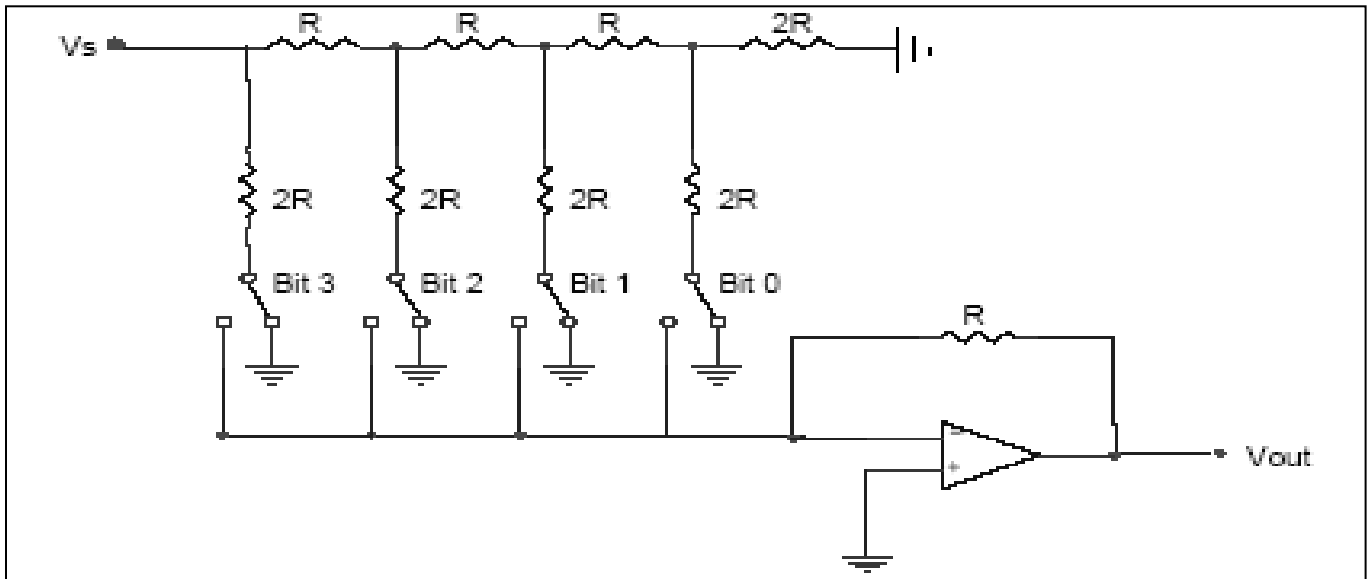


Figure 2. DAC by R-2R Ladder

If the bit is high, the corresponding switch is connected to the inverting input of the op-amp. If the bit is low, the corresponding switch is connected to ground.

b_n means Bit n , hence;

If bit n is set, $b_n=1$

If bit n is clear, $b_n=0$

For a 4-Bit R-2R Ladder, output is equal to;

$$V_{\text{out}} = -V_{\text{ref}} \left(b_3 \frac{1}{2} + b_2 \frac{1}{4} + b_1 \frac{1}{8} + b_0 \frac{1}{16} \right)$$

For general n -Bit R-2R Ladder, output is equal to;

$$V_{\text{out}} = -V_{\text{ref}} \sum_{i=1}^n b_{n-i} \frac{1}{2^i}$$

Experimental Procedure:

- 1) Construct the circuit in Figure 1 and fill in Table 1 (use 10k resistors in parallel configurations).
- 2) Construct the circuit in Figure 3 and fill in Table 2.

Table 1. Results for the circuit in Figure 1.

<i>Sw0</i>	<i>Sw1</i>	<i>Sw2</i>	<i>Sw3</i>	<i>i_{out}</i>	<i>v_o</i>
<i>closed</i>	<i>open</i>	<i>open</i>	<i>open</i>		
<i>open</i>	<i>closed</i>	<i>open</i>	<i>open</i>		
<i>closed</i>	<i>closed</i>	<i>open</i>	<i>open</i>		
<i>open</i>	<i>open</i>	<i>closed</i>	<i>open</i>		
<i>closed</i>	<i>open</i>	<i>closed</i>	<i>open</i>		
<i>open</i>	<i>closed</i>	<i>closed</i>	<i>open</i>		
<i>closed</i>	<i>closed</i>	<i>closed</i>	<i>open</i>		
<i>open</i>	<i>open</i>	<i>open</i>	<i>open</i>		
<i>closed</i>	<i>open</i>	<i>open</i>	<i>closed</i>		
<i>open</i>	<i>closed</i>	<i>open</i>	<i>closed</i>		
<i>closed</i>	<i>closed</i>	<i>open</i>	<i>closed</i>		
<i>open</i>	<i>open</i>	<i>closed</i>	<i>closed</i>		
<i>closed</i>	<i>open</i>	<i>closed</i>	<i>closed</i>		
<i>open</i>	<i>closed</i>	<i>closed</i>	<i>closed</i>		
<i>closed</i>	<i>closed</i>	<i>closed</i>	<i>closed</i>		

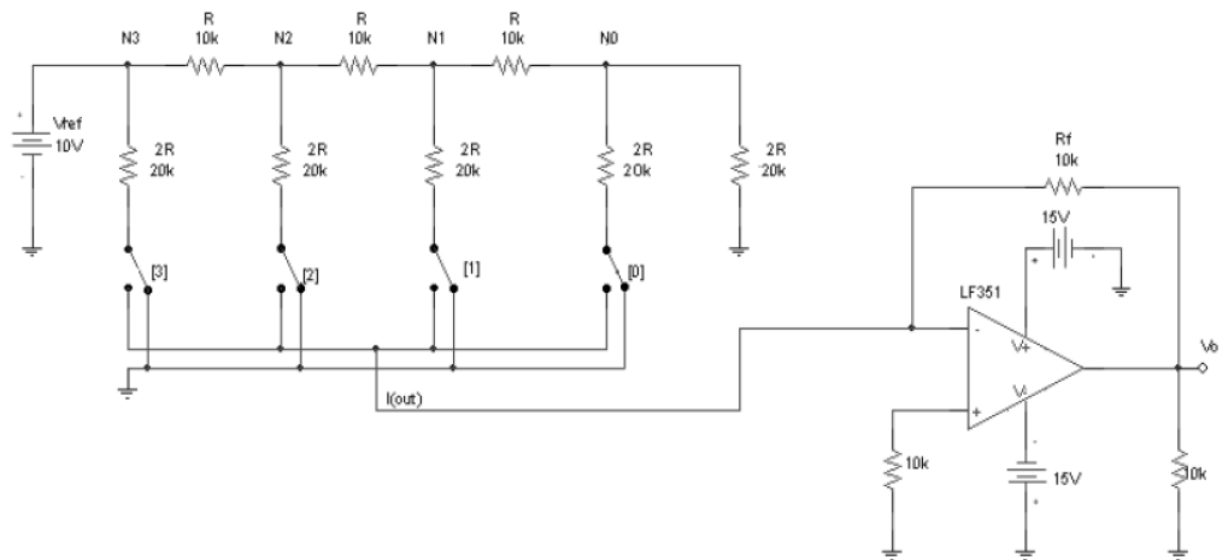


Figure 3. R-2R ladder circuit to be constructed

Table 2. Results for the circuit in Figure 3.

<i>Sw0</i>	<i>Sw1</i>	<i>Sw2</i>	<i>Sw3</i>	i_{out}	v_o
<i>closed</i>	<i>open</i>	<i>open</i>	<i>open</i>		
<i>open</i>	<i>closed</i>	<i>open</i>	<i>open</i>		
<i>closed</i>	<i>closed</i>	<i>open</i>	<i>open</i>		
<i>open</i>	<i>open</i>	<i>closed</i>	<i>open</i>		
<i>closed</i>	<i>open</i>	<i>closed</i>	<i>open</i>		
<i>open</i>	<i>closed</i>	<i>closed</i>	<i>open</i>		
<i>closed</i>	<i>closed</i>	<i>closed</i>	<i>open</i>		
<i>open</i>	<i>open</i>	<i>open</i>	<i>open</i>		
<i>closed</i>	<i>open</i>	<i>open</i>	<i>closed</i>		
<i>open</i>	<i>closed</i>	<i>open</i>	<i>closed</i>		
<i>closed</i>	<i>closed</i>	<i>open</i>	<i>closed</i>		
<i>open</i>	<i>open</i>	<i>closed</i>	<i>closed</i>		
<i>closed</i>	<i>open</i>	<i>closed</i>	<i>closed</i>		
<i>open</i>	<i>closed</i>	<i>closed</i>	<i>closed</i>		
<i>closed</i>	<i>closed</i>	<i>closed</i>	<i>closed</i>		

Conclusion : Compare ideal and experimental results. What is the rate of the difference? Explain its reasons.